

S. NO.: 227

BATCH: 2009-18, 2016

Reg. No.:

END OF SEMESTER EXAMINATIONS, APRIL / MAY - 2017

DIGITAL COMPUTER FUNDAMENTALS

SUBJECT CODE : 09UACT04

MAJOR : B.Sc. (CT)

TIME : 3 HOURS

SEMESTER : II

MAX. MARKS: 75

SECTION A – (5 X 2 = 10)

Answer ALL the Questions:

1. What is the use of gray code?
2. What is the purpose of BCD adder?
3. Write the function of a decoder.
4. What is meant by Handshaking?
5. List down any four logic micro operations.

SECTION B – (5 X 4 = 20)

Answer ALL the Questions:

6. a) Explain the following with an example.
 - i) Hexadecimal to binary conversion
 - ii) Binary to Hexadecimal conversion
 - iii) Hexadecimal to decimal conversion
 - iv) Decimal to Hexadecimal conversion

(OR)

 - b) Explain the fundamentals of number system.
7. a) Write short note on parallel binary adder.

(OR)

- b) Explain the NAND, NOR and Ex-OR gates with Truth Table.
- 8. a) Draw and explain the 4-bit register.

(OR)

- b) Illustrate on Ripple counters.
- 9. a) Write brief note on Input / output Interface.

(OR)

- b) What are the types of buses? Explain them.
- 10. a) Explain the register transfer and micro operations.

(OR)

- b) Illustrate on various addressing modes used in microprocessor.

SECTION C – (3 X 15 = 45)

Answer any THREE Questions:

11. Draw fundamental blocks of a computer and explain each of them.
12. Discuss the full adder with neat diagram.
13. Describe JK and JK Master – Slave flip flop with its truth table.
14. Briefly explain about asynchronous data transfer.
15. Explain the process of CPU-IOP communication.
