

[Empty box for registration number]

END OF SEMESTER EXAMINATIONS, NOVEMBER - 2017  
DIGITAL ELECTRONICS, MICROPROCESSOR AND MICROCONTROLLERS  
SUBJECT CODE: 12UAPH07

12

MAJOR: B.Sc., (Physics)/Physics (CAD)  
TIME : 3 HOURS

SEMESTER: V  
MAX.MARKS: 75

SECTION - A ( 10 X 1 = 10 )

Answer ALL the Questions:

1. Convert hexa decimal number to binary  $(7A23)_{16} = ( )_2$ 
  - a)  $(0111 1010 0010 0011)_2$
  - b)  $(1000 0101 1101 1100)_2$
  - c)  $(111 1010 10 11)_2$
  - d)  $(0111 1010 0011 0010)_2$
2. Write the abbreviation of BCD
  - a) Basic Code Digits
  - b) Binary Coded Decimal
  - c) Binary Coded Digits
  - d) Basic Code Decimal
3. When both the inputs of J and K is HIGH, the output action is
  - a) Set
  - b) Reset
  - c) Last State
  - d) Toggle
4. Four adjacent is in K-map is called
  - a) Pair
  - b) Quad
  - c) Octet
  - d) Implicant
5. Expand PIPO
  - a) Parallel in Pulse Out
  - b) Parallel in Parallel Out
  - c) Pulse in Pulse Out
  - d) Pulse in Parallel Out
6. To construct mod-3 counter we need \_\_\_\_\_ number of flip flops.
  - a) Three
  - b) Two
  - c) Four
  - d) Only one
7. MVI stands for
  - a) Move among registers
  - b) Move immediate data to registers
  - c) Move the Information
  - d) Move the address.
8. Accumulator register is a \_\_\_\_\_ bit register
  - a) 8-Bit
  - b) 16-Bit
  - c) 6-Bit
  - d) 10-Bit
9. 8056 Microcontroller is a \_\_\_\_\_
  - a) 8-Bit CPU
  - b) 10-Bit CPU
  - c) 16-Bit CPU
  - d) 32 Bit CPU
10. XCH A, < Byte > means
  - a) Exchange accumulator with byte variable
  - b) Exchange register
  - c) HL Pair
  - d) BC Pair

**SECTION - B ( 5 X 4 = 20 )****Answer ALL the Questions:**

11. a) Perform (i)  $11011 - 10010$  (ii)  $101 \times 11$

(OR)

- b) Explain OR gate with diagram and truth table.

12. a) Discuss the concept of half Subtractor with diagram and truth table.

(OR)

- b) What is T flip flop? Explain its concept .

13. a) Discuss the concept of 4-Bit Asynchronous counter.

(OR)

- b) What is a shift register? Discuss its construction.

14. a) Write any two types of addressing modes. Explain with example.

(OR)

- b) Write a simple program in 8085 to Subtract 2 8-Bit numbers.

15. a) Explain timer flag interrupt.

(OR)

- b) Differentiate between a microcontroller and a microprocessor.

**SECTION - C ( 5 X 9 = 45 )****Answer ALL the Questions:**

16. a) Prove that NAND as universal gate with neat diagram and truth table.

(OR)

- b) (i) Perform  $(649)_{10} = (?)_8$   $(10110)_2 = (?)_{10}$  (ii) Write a short note on 8421 code

17. a) Explain the concept of full adder circuit with neat sketch and truth table.

(OR)

- b) How master slave flip flop works? Explain with neat sketch.

18. a) Briefly explain the procedure for serial-in-paraller out shift register with neat sketch.

(OR)

- b) Construct Mod-6 counter -Explain.

19. a) Explain in detail the architecture of 8085 microprocessor.

(OR)

- b) Explain types of data transfer instructions with example and symbolic representation .

20. a) In detail explain the block diagram of Micro Controller.

(OR)

- b) Explain arithmetic instructions with example.

\*\*\*\*\*