

12

END OF SEMESTER EXAMINATIONS, NOVEMBER - 2017
DIGITAL ELECTRONICS, MICROPROCESSOR AND MICROCONTROLLERS
SUBJECT CODE: 12UAPH07

MAJOR: B.Sc., (Physics)/Physics (CAD)
TIME : 3 HOURS

SEMESTER: V
MAX.MARKS: 75

SECTION - A (10 X 1 = 10)

Answer ALL the Questions:

1. Convert hexa decimal number to binary $(7A23)_{16} = ()_2$
 - a) $(0111\ 1010\ 0010\ 0011)_2$
 - b) $(1000\ 0101\ 1101\ 1100)_2$
 - c) $(111\ 1010\ 10\ 11)_2$
 - d) $(0111\ 1010\ 0011\ 0010)_2$
2. Write the abbreviation of BCD
 - a) Basic Code Digits
 - b) Binary Coded Decimal
 - c) Binary Coded Digits
 - d) Basic Code Decimal
3. When both the inputs of *J* and *K* is *HIGH*, the output action is
 - a) Set
 - b) Reset
 - c) Last State
 - d) Toggle
4. Four adjacent is in *K-map* is called
 - a) Pair
 - b) Quad
 - c) Octet
 - d) Implicant
5. Expand PIPO
 - a) Parallel in Pulse Out
 - b) Parallel in Parallel Out
 - c) Pulse in Pulse Out
 - d) Pulse in Parallel Out
6. To construct mod-3 counter we need _____ number of flip flops.
 - a) Three
 - b) Two
 - c) Four
 - d) Only one
7. MVI stands for
 - a) Move among registers
 - b) Move immediate data to registers
 - c) Move the Information
 - d) Move the address.
8. Accumulator register is a _____ bit register
 - a) 8-Bit
 - b) 16-Bit
 - c) 6-Bit
 - d) 10-Bit
9. 8056 Microcontroller is a _____
 - a) 8-Bit CPU
 - b) 10-Bit CPU
 - c) 16-Bit CPU
 - d) 32 Bit CPU
10. XCH A, < Byte > means
 - a) Exchange accumulator with byte variable
 - b) Exchange register
 - c) HL Pair
 - d) BC Pair

SECTION – B (5 X 4 = 20)**Answer ALL the Questions:**

11. a) Perform (i) $11011 - 10010$ (ii) 101×11

(OR)

- b) Explain OR gate with diagram and truth table.

12. a) Discuss the concept of half Subtractor with diagram and truth table.

(OR)

- b) What is T flip flop? Explain its concept .

13. a) Discuss the concept of 4-Bit Asynchronous counter.

(OR)

- b) What is a shift register? Discuss its construction.

14. a) Write any two types of addressing modes. Explain with example.

(OR)

- b) Write a simple program in 8085 to Subtract 2 8-Bit numbers.

15. a) Explain timer flag interrupt.

(OR)

- b) Differentiate between a microcontroller and a microprocessor.

SECTION – C (5 X 9 = 45)**Answer ALL the Questions:**

16. a) Prove that NAND as universal gate with neat diagram and truth table.

(OR)

- b) (i) Perform $(649)_{10} = (?)_8$ $(10110)_2 = (?)_{10}$ (ii) Write a short note on 8421 code

17. a) Explain the concept of full adder circuit with neat sketch and truth table.

(OR)

- b) How master slave flip flop works? Explain with neat sketch.

18. a) Briefly explain the procedure for serial-in-paraller out shift register with neat sketch.

(OR)

- b) Construct Mod-6 counter –Explain.

19. a) Explain in detail the architecture of 8085 microprocessor.

(OR)

- b) Explain types of data transfer instructions with example and symbolic representation .

20. a) In detail explain the block diagram of Micro Controller.

(OR)

- b) Explain arithmetic instructions with example.
